

HSpice simulation tutorial in Linux:

- 1) Create a netlist using any text editor and save it as [filename].sp.
You can include the model file by using 'INC [path to model file] ', or you can copy the model file and insert it into the netlist directly (not preferred).
The model file for this course – par0.18um.net is included in this folder. Please save it and note its path so that you can use it in netlists.
- 2) Run a Star-Hspice analysis in the terminal by typing:
hspice [filename].sp >! [filename].lis

If you use only '>' and [filename].lis already exists, message appears that '[filename].lis: File exists',
but '>!' does not lead to this problem.

When the run finishes successfully, the Star-Hspice displays
>info: ***** hspice job concluded

If not, it will display


>info: ***** hspice job aborted

Then you need to examine the syntax of the input netlist file.


- 3) Open the [filename].lis to view the simulation results.
- 4) In the terminal, type 'scope' to open CosmosScope to view the waveforms.
'File' --> 'Open'-->'Plotfiles'-->'Files of type [HSPICE (*.tr*, *.ac, *.sw*, *.ft*)]'

Example 1: NMOS

Testbench for NMOS is shown as below:

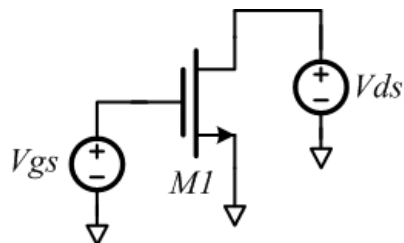

- a) Netlist: NMOS.sp

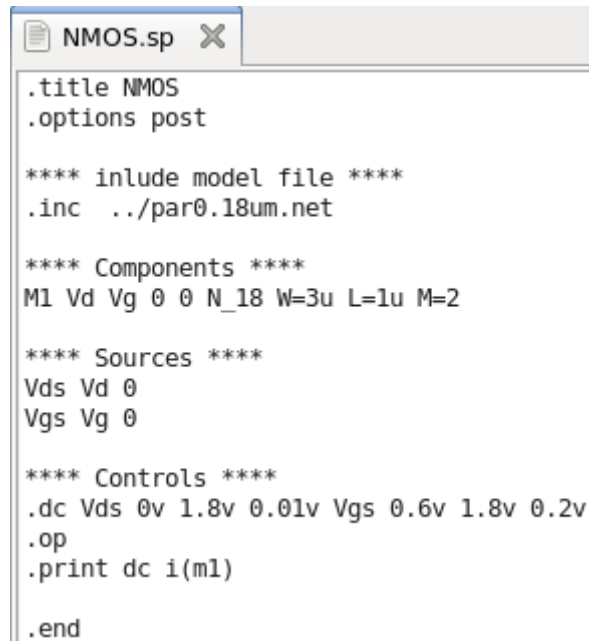

```
.title NMOS
.options post


**** include model file ****
.inc ../par0.18um.net

**** Components ****
M1 Vd Vg 0 0 N_18 W=3u L=1u M=2

**** Sources ****
Vds Vd 0
Vgs Vg 0

**** Controls ****
.dc Vds 0v 1.8v 0.01v Vgs 0.6v 1.8v 0.2v
.op
.print dc i(m1)
.end
```

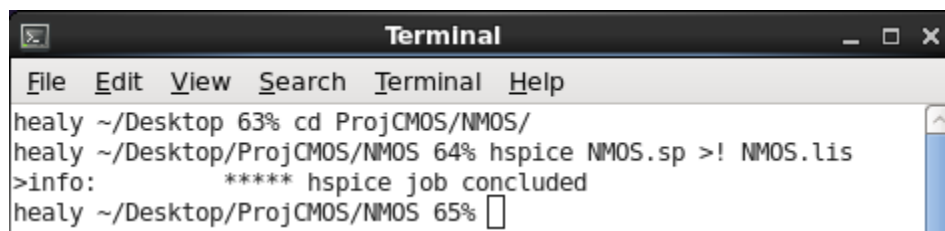
b) Move to the directory where [filename].sp exists and start Hspice to simulate



```
Terminal
File Edit View Search Terminal Help
healy ~/Desktop 63% cd ProjCMOS/NMOS/
healy ~/Desktop/ProjCMOS/NMOS 64% hspice NMOS.sp >! NMOS.lis
>info:          ***** hspice job concluded
healy ~/Desktop/ProjCMOS/NMOS 65%
```


c) View the waveform using CosmosScope

healy ~/Desktop/ProjCMOS/NMOS 65% scope

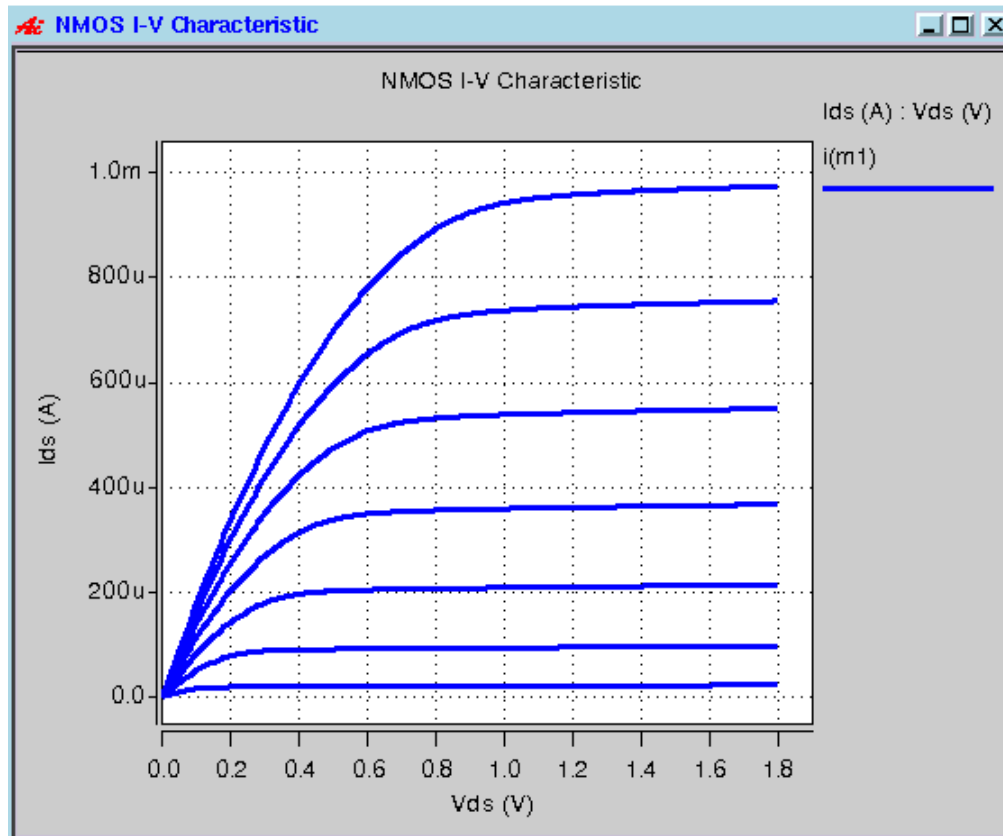


1. PMOS

Testbench for PMOS is shown as below:

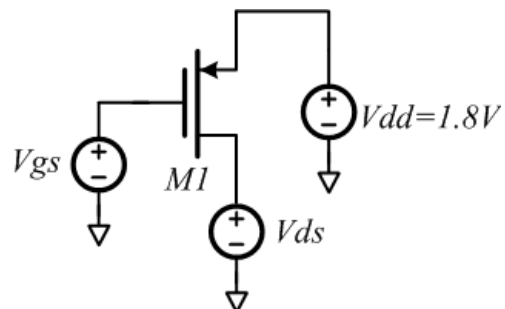

a) Netlist: PMOS.sp

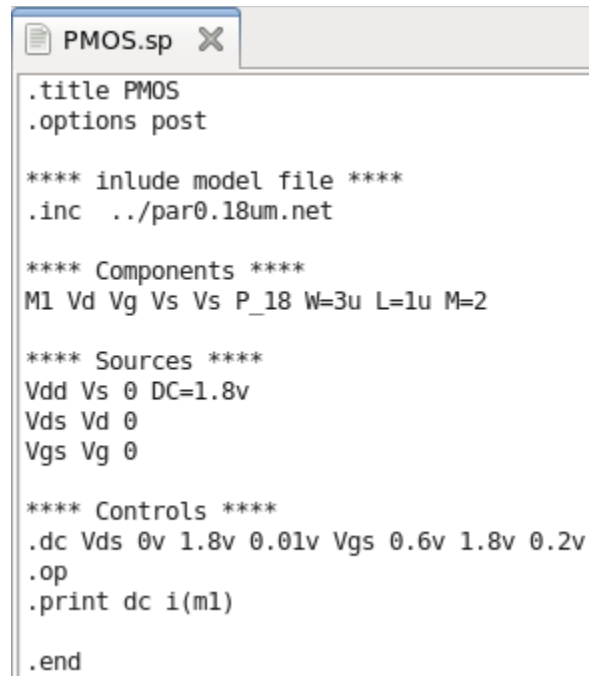

```
.title PMOS
.options post

**** include model file ****
.inc ../par0.18um.net


**** Components ****
M1 Vd Vg Vs Vs P_18 W=3u L=1u M=2

**** Sources ****
Vdd Vs 0 DC=1.8v
Vds Vd 0
Vgs Vg 0

**** Controls ****
.dc Vds 0v 1.8v 0.01v Vgs 0.6v 1.8v 0.2v
.op
.print dc i(m1)


.end
```

b) Start Hspice to simulate

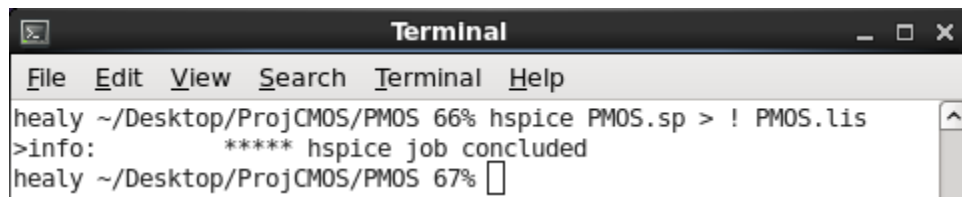


```
Terminal
File Edit View Search Terminal Help
healy ~/Desktop/ProjCMOS/PMOS 66% hspice PMOS.sp > ! PMOS.lis
>info:          ***** hspice job concluded
healy ~/Desktop/ProjCMOS/PMOS 67% █
```

c) View the waveform

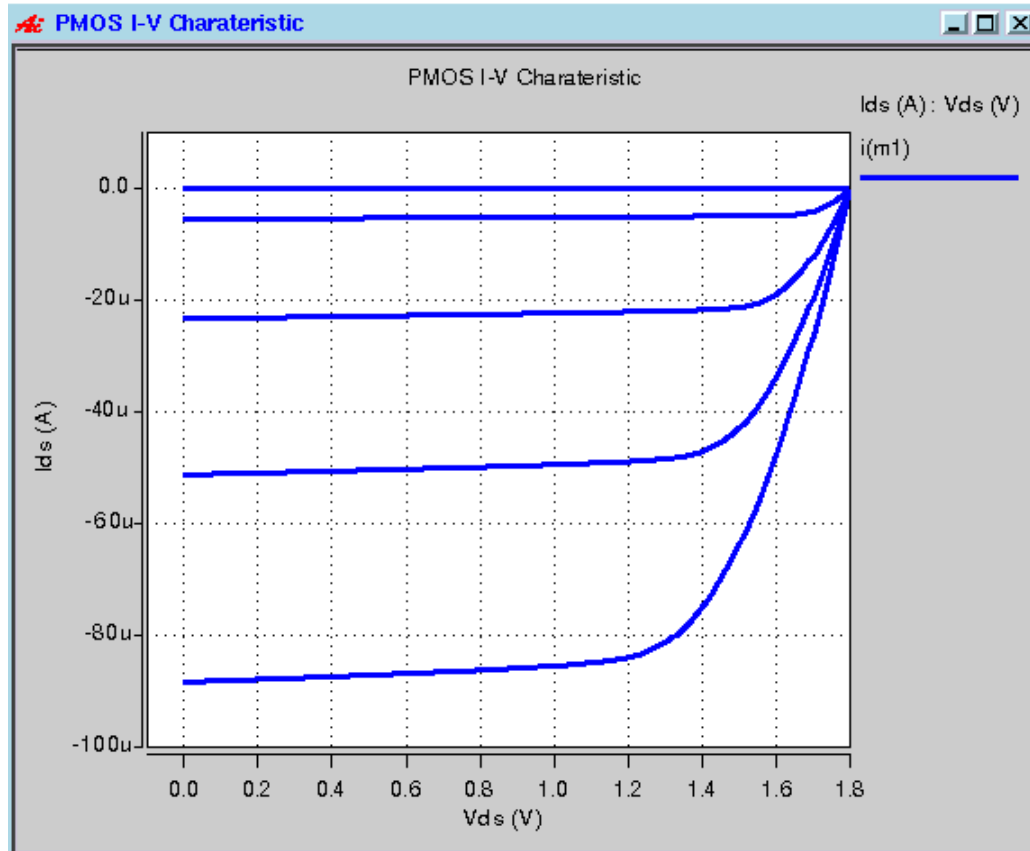

2. Common-Source Amplifier with Active Load

Testbench for PMOS is shown as below:

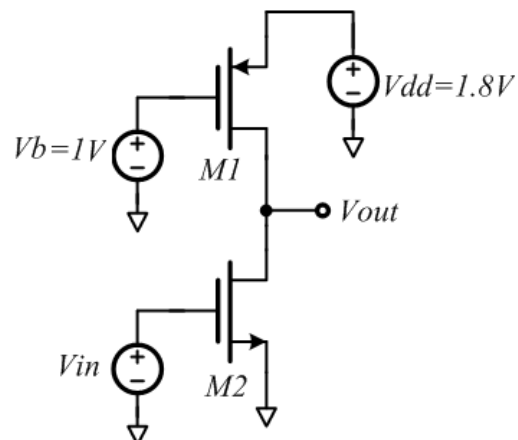

a) Netlist: CommSource.sp

```

CommSource.sp
.title CommSource
.options post

**** include model file ****
.inc ../par0.18um.net

**** Components ****
M1 Vout Vb vd Vd P_18 W=3u L=1u M=2
M2 Vout Vg 0 0 N_18 W=3u L=1u M=2

**** Sources ****
Vdd Vd 0 DC=1.8v
Vbb Vb 0 DC=1v
Vin Vg 0

**** Controls ****
.dc Vin 0v 1.8v 0.01v
.op
.print dc v(Vout)

.end

```

b) View the waveform

